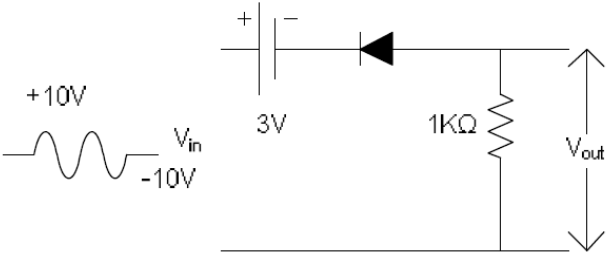



BE Semester – III (INSTRUMENTATION AND CONTROL ENGG.)

Question Bank

(IC 304 BASIC ELECTRONICS)

All questions carry equal marks(10 marks)

Q-1	What is key characteristic of Tunnel Diode? Write a short note on it.
Q-2	Explain the difference between conductor, insulator and semiconductors with energy diagrams.
Q-3	Draw the symbols: 1) Current regulator diode, 2) Schottky diode, 3) Laser diode, 4)Photo diode, 5) Tunnel Diode, 6) LED, 7) PNP Transistor, 8) NPN Transistor, 9) FET, 10) MOSFET
Q-4	Explain basic transistor amplifier circuit. Derive voltage gain A_v . If $R_C = 1\text{ k}\Omega$ and $r_e' = 50\ \Omega$, what is A_v ?
Q-5	Using the diagram, explain cutoff, saturation and DC load line characteristic curves.
Q-6	Explain voltage divider bias and derive I_C and V_{CE} .
Q-7	Explain Class A, Class B and Class C amplifier basic operations.
Q-8	Explain full-wave rectifier by using center-tap and derive the expression for D.C. voltage, D.C. current, efficiency and ripple factor.
Q-9	Explain voltage doubler circuit in detail.
Q-10	Explain the zener breakdown characteristics and its application as a voltage regulator in detail.
Q-11	With the help of neat sketch explain the construction of FET. Also discuss the FET static characteristics.
Q-12	Explain the working of Depletion type and Enhancement type MOSFET.
Q-13	Write a short note on Varactor Diode.
Q-14	What is Biasing? What are various biasing methods for BJT? Give circuit diagrams for each of them.
Q-15	Define h-parameters of transistor. Find A_v , A_i , Z_i , Z_o for the CE amplifier in terms of h-parameter.
Q-16	Write a short note on class A power amplifier in detail.
Q-17	Explain transformer-coupled class B push-pull amplifier circuits.
Q-18	Explain V-I Characteristic of Zener diode and explain application of zener diode as a Clipper.
Q-19	Determine the o/p voltage waveform for the figures given below: 

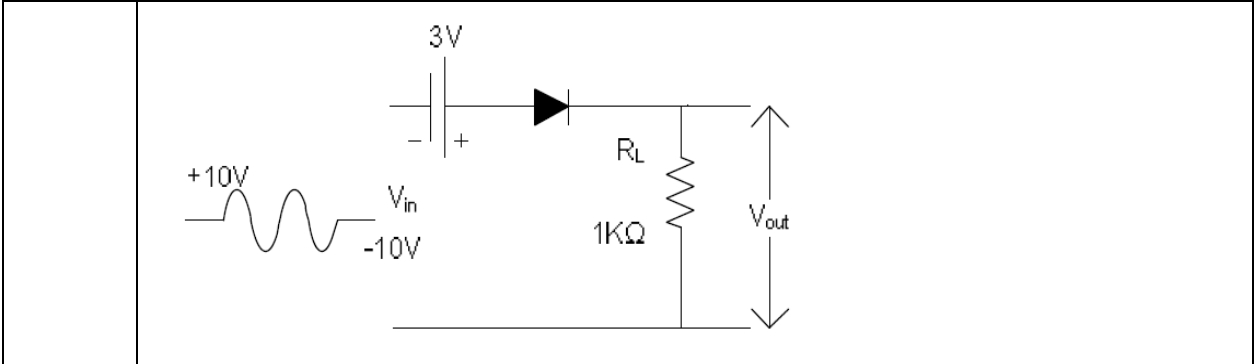


Q-20 What is CMOS? Explain CMOS Inverter.

Q-21 Explain A.C. resistance and D.C. resistance with respect to Diodes.

Q-22 Explain V-I Characteristic of photodiode.


Q-23 Explain the Clamper circuits with waveforms.


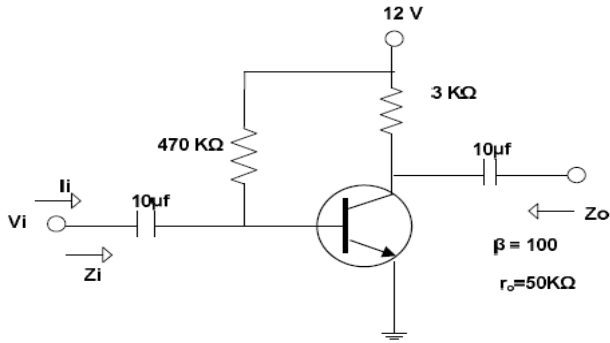
Q-24 For the network of figure determine r_e . Calculate Z_i , Z_o , A_v .




Q-25 Give constructional details of JFET and give its characteristics. Why FET is called Voltage controlled device?

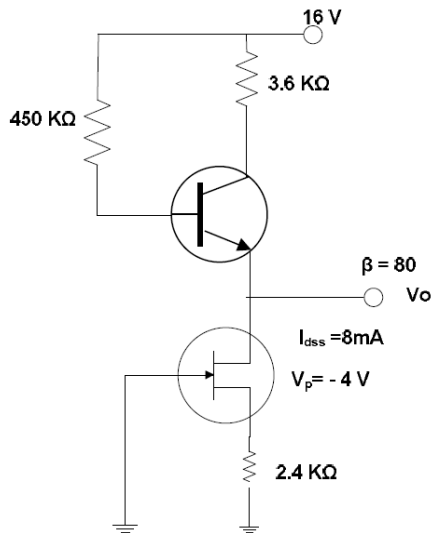Q-26 Determine V_o for the circuit given below:



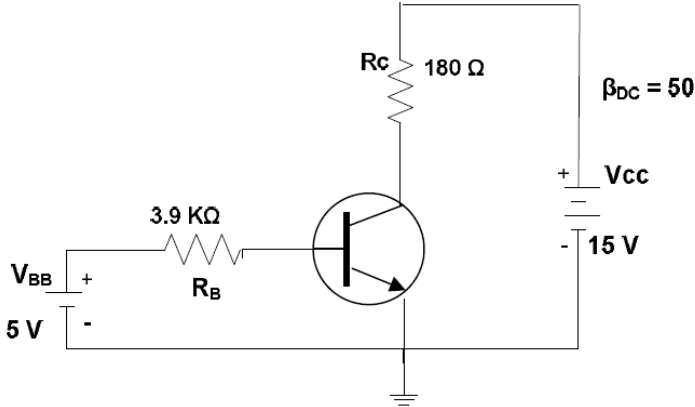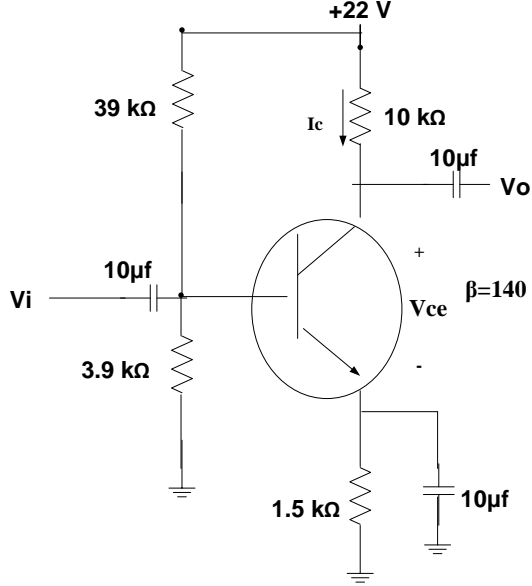Q-27	<p>Find V_{ce}, V_{be} & V_{cb} of the circuit given below:</p> 
Q-28	<p>Explain basic operation and characteristic of n-channel depletion type MOSFET with necessary diagram.</p>
Q-29	<p>Determine V_{CE} and I_C for figure given below:</p> 
Q-30	<p>Explain bohr's postulate in detail.</p>
Q-31	<p>Write a short note on CMOS.</p>
Q-32	<p>Draw and explain the input and output characteristic of CB configuration.</p>
Q-33	<p>For a certain transistor, $I_C = 5.255 \text{ mA}$, $I_B = 100 \mu\text{A}$, and $I_{CBO} = 5 \mu\text{A}$ (i) calculate α, β and I_E (ii) Determine the new level of I_B required to make $I_C = 15 \text{ mA}$</p>
Q-34	<p>Write a short note on phototransistor.</p>
Q-35	<p>Explain Hall effect with neat sketch. Discuss how to measure charge density and mobility for a given specimen of semiconductor using Hall Effect?</p>

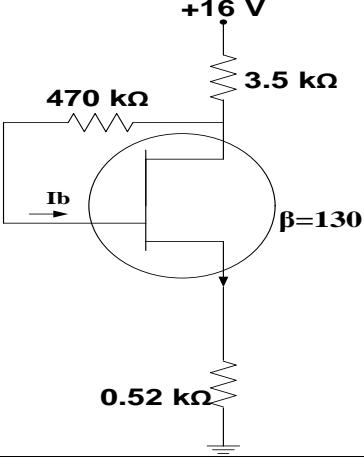Q-36	Describe the types of clippers. Explain positive clippers with circuit diagram in detail.
Q-37	Give the difference between BJT and MOSFET.
Q-38	<p>For the collector feedback configuration, given in figure, find out the values of I_B, I_C and V_C.</p> 
Q-39	Draw Emitter follower circuit. Obtain Hybrid equivalent circuit and derive expression for current gain.
Q-40	Explain Testing methods of Transistors in detail.